

# Lab 3 - DLX Fetch

Nate Herbst  
A02307138  
Nathan Walker  
A02364124

## Introduction

This project required making the fetch stage out of the 5 stages for the DLX processor. This stage has several components including: registers, Muxes, adders, and ROMs. This project entails incrementing the program counter so that the decode stage would receive the instruction at the current PC value, and the PC + 1 value. With the option to have a jump address selected from the execute stage of the processor.

## Procedure

### Modular Systems:

- We started off by making each block that would match the blocks we had made in our block diagram. (See Figure 1)
- We then tied them together
- We then made each test bench to verify each smaller piece of the bigger puzzle. (See Figures 2-4)
- Created `_pkg` files for each component to ease the use of them in later labs if needed

### Challenges and Solutions:

- The primary difficulty lay in simulating the top-level `fetch.vhd` file within Questa. Lacking the complete soft-core processor, specifically the `Decode` and `Execute` stages, made it challenging to accurately model the source of the next program counter or jump instruction. This required significant effort to determine the correct clock cycle delays, but we successfully developed the necessary testbench to achieve a working simulation.

# Results

The final implementation showed us that the fetch stage can correctly increment the PC and grab correct instructions. It can also be selected to jump to a certain instruction address and properly increment the counter from the jump. The Fetch stage was made in a modular fashion so in the future it can be easily changed and portions can easily be ported to other sections.

## Figures

 


Figure 1: First Initial Block diagram for all the blocks we needed to implement and link together

 


Figure 2: Ripple adder simulation

 


Figure 3: Register simulation



Figure 4: MUX simulation

 


Figure 5: Sim snapshot of the fetch stage working

## Conclusion

This lab provided valuable insights into the workflow on implementing different stages of a processor. This lab will help us in the future labs as we have a better understanding of how to pipeline the data and when and where to register the data. It has been a fun experience and we are learning a lot of hardware design flow through this.

# Appendix

## fetch.vhd (top level file)

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

library work;
--use work.register_pkg.all;
--use work.MUX_pkg.all;
--use work.ripple_adder_pkg.all;

entity fetch is
    generic (
        N      : integer := 10;
        M      : integer := 32
    );
    port (
        jump_addr   : in      std_logic_vector(N-1 downto 0);
        pc_select   : in      std_logic;
        rst         : in      std_logic;
        clk         : in      std_logic;
        decode_addr : out std_logic_vector(N-1 downto 0);
        instruction : out std_logic_vector(M-1 downto 0)
    );
end entity;

architecture component_list of fetch is

    signal new_addr   : std_logic_vector(N-1 downto 0) := (others => '0');
    signal addr       : std_logic_vector(N-1 downto 0) := (others => '0');
    signal sum        : std_logic_vector(N-1 downto 0) := (others => '0');
    signal C_DUMMY    : std_logic;

    constant LSB_ONE  : std_logic_vector(N-1 downto 0) :=
        (N-2 downto 0 => '0') & '1';
```

```

constant ZERO      :    std_logic := '0';

begin

    PC_counter  :    entity work.reggi
        generic map(
            N => 10
        )
        port map(
            data_in      => new_addr,
            rst          =>  rst,
            clk          =>  clk,
            data_out     =>  addr
        );

    ADDER        :    entity work.ripple_adder
        generic map(
            N => 10
        )
        port map(
            A           => addr,
            B           => LSB_ONE,
            C_in        => ZERO,
            SUM => sum,
            C_out => C_DUMMY
        );

    MUXXY        :    entity work.MUX
        generic map(
            N => 10
        )
        port map(
            A           =>  jump_addr,
            B           => sum,
            S           => pc_select,
            OUTPUT=>    new_addr
        );

    MUX_REGISTER  :    entity work.reggi
        generic map(

```

```

        N => 10
    )
    port map(
        data_in => new_addr,
        rst      => rst,
        clk      => clk,
        data_out  => decode_addr
    );

    --insert IP ROM device with .mif file
    IMEM      : entity work.factorial_ROM
    port map(
        address => addr,
        clock   => clk,
        q       => instruction
    );

end architecture component_list;

```

## tb\_fetch.vhd

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity tb_fetch is
end tb_fetch;

architecture behavioral of tb_fetch is

    component fetch
        generic (
            N      : integer := 10;
            M      : integer := 32
        );
        port (
            jump_addr    : in      std_logic_vector(N-1 downto 0);
            pc_select    : in      std_logic;
            rst           : in      std_logic;

```

```

        clk          :    in          std_logic;
        decode_addr  :    out std_logic_vector(N-1 downto 0);
        instruction  :    out std_logic_vector(M-1 downto 0)
    );
end component fetch;

-- Clock
signal clk : std_logic;
constant CLK_PERIOD : time := 10 ns;

-- Testbench signals
signal tb_jump_addr : std_logic_vector(9 downto 0) := (others => '0');
signal tb_pc_select : std_logic := '0';
signal tb_rst       : std_logic := '1';
signal tb_decode_addr : std_logic_vector(9 downto 0);
signal tb_instruction : std_logic_vector(31 downto 0);

begin

    -- Instantiate the fetch stage
    uut : fetch
        generic map (
            N => 10,
            M => 32
        )
        port map(
            jump_addr    => tb_jump_addr,
            pc_select    => tb_pc_select,
            rst          => tb_rst,
            clk          => clk,
            decode_addr  => tb_decode_addr,
            instruction  => tb_instruction
        );

    -- Clock process
    clk_process : process
    begin
        clk <= '0';
        wait for CLK_PERIOD / 2;
        clk <= '1';
    end process;
end;

```



```

        wait for CLK_PERIOD / 2;
    end process;

    -- Stimulus process for factorial program
    stm_process : process
    begin
        -- 1. Reset the system to start at address 0
        tb_rst <= '1';
        wait for CLK_PERIOD * 2;
        tb_rst <= '0';
        wait for CLK_PERIOD;

        -- 2. Fetch instructions 0x000 through 0x004. At 0x004 (BEQZ),
assume branch not taken.
        tb_pc_select <= '0';
        wait for CLK_PERIOD * 5;

        -- 3. At PC=0x005, instruction is JAL factorial (0x008). Jump
there.
        wait for CLK_PERIOD*2;
        tb_pc_select <= '1';
        tb_jump_addr <= "0000001000"; -- Jump to address 0x008
        wait for CLK_PERIOD;
        tb_pc_select <= '0';
        wait for CLK_PERIOD;

        -- 4. Fetch 0x008, 0x009, 0x00A, 0x00B.
        wait for CLK_PERIOD * 4;

        -- 5. At PC=0x00C, instruction is SUBI. Fetch it.
        wait for CLK_PERIOD;

        -- 6. At PC=0x00D, instruction is BNEZ multiply_loop (0x00B).
Simulate branch taken.
        tb_pc_select <= '1';
        tb_jump_addr <= "0000001011"; -- Jump to address 0x00B
        wait for CLK_PERIOD;
        tb_pc_select <= '0';
        wait for CLK_PERIOD;
    end process;

```

```

-- 7. We are back at 0x00B. Fetch 0x00B, 0x00C.
wait for CLK_PERIOD * 2;

-- 8. At PC=0x00D, BNEZ again. This time, simulate branch NOT
taken.
wait for CLK_PERIOD;

-- 9. At PC=0x00E, instruction is SW. Fetch it.
wait for CLK_PERIOD;

-- 10. At PC=0x00F, instruction is JR R31. Return address was
0x005+1=0x006. Jump there.
tb_pc_select <= '1';
tb_jump_addr <= "0000000110"; -- Jump to address 0x006
wait for CLK_PERIOD;
tb_pc_select <= '0';
wait for CLK_PERIOD;

-- 11. At PC=0x006, instruction is SUBI. Fetch it.
wait for CLK_PERIOD;

-- 12. At PC=0x007, instruction is J loop (0x004). Jump there.
tb_pc_select <= '1';
tb_jump_addr <= "0000000100"; -- Jump to address 0x004
wait for CLK_PERIOD;
tb_pc_select <= '0';
wait for CLK_PERIOD;

-- 13. At PC=0x004, BEQZ again. This time, simulate branch TAKEN to
'done' (0x010).
tb_pc_select <= '1';
tb_jump_addr <= "0000010000"; -- Jump to address 0x010
wait for CLK_PERIOD;
tb_pc_select <= '0';
wait for CLK_PERIOD;

-- 14. At PC=0x010, instruction is J done (itself). Fetch it.
wait for CLK_PERIOD * 2;

wait;

```

```
end process;  
  
end architecture behavioral;
```

## ripple\_adder.vhd

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
library work;  
use work.full_adder_pkg.all;  
  
entity ripple_adder is  
    generic (  
        N : integer := 10  
    );  
    port (  
        A      : in std_logic_vector(N-1 downto 0);  
        B      : in std_logic_vector(N-1 downto 0);  
        C_in   : in std_logic;  
        SUM    : out std_logic_vector(N-1 downto 0);  
        C_out  : out std_logic  
    );  
end entity ripple_adder;  
  
architecture rtl of ripple_adder is  
  
    signal C      : std_logic_vector(N downto 0);  
  
begin  
  
    C(0) <= C_in;  
  
    gen_adders : for i in 0 to N-1 generate  
        FA : entity work.full_adder  
            port map(  
                A      => A(i),  
                B      => B(i),
```

```

        C_in    => C(i),
        SUM     => SUM(i),
        CARRY   => C(i+1)
    );
end generate gen_adders;

C_out <= C(N);

end architecture rtl;

```

## register.vhd

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity reggi is
    generic (
        N      : integer := 10
    );
    port (
        data_in : in  std_logic_vector(N-1 downto 0);
        rst     : in  std_logic;
        clk     : in  std_logic;
        data_out : out std_logic_vector(N-1 downto 0)
    );
end entity reggi;

architecture behavioral of reggi is

    signal output_data : std_logic_vector(N-1 downto 0)
        := (others => '0');

begin

    data_out <= output_data;
    process(clk) begin
        if rising_edge(clk) then
            if rst = '1' then

```

```

        output_data <= (others => '0');
    else
        output_data <= data_in;
    end if;
end if;
end process;

end architecture behavioral;

```

## MUX.vhd

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity MUX is
    generic (
        N : integer := 10
    );
    port (
        A      : in      std_logic_vector(N-1 downto 0);
        B      : in      std_logic_vector(N-1 downto 0);
        S      : in      std_logic;
        OUTPUT: out      std_logic_vector(N-1 downto 0)
    );
end entity MUX;

architecture rtl of MUX is

begin

    OUTPUT <= A when S = '1' else B;

end architecture rtl;

```